




Digital Electronics

- Part I: Digital Principle -

Dr. Lê Dũng

Department of Electronics and Computer System (C9-401)
 School of Electronics and Telecommunications
 Hanoi University of Science and Technology
 Email: ledung-fet@mail.hut.edu.vn

Part I: Digital Principles - Overview

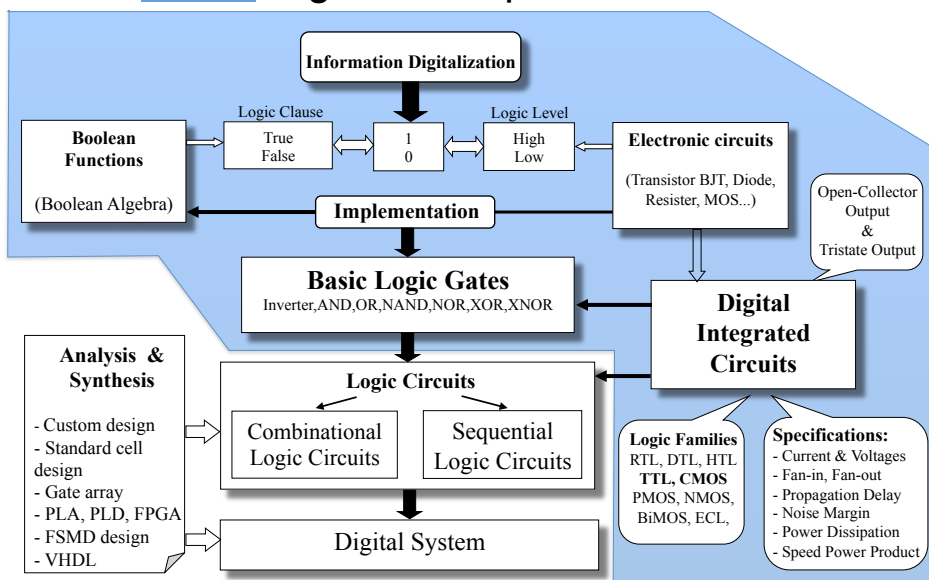

Part I: Digital Principles - Contents

Chapter 1 : Binary system and Binary Codes

Chapter 2 : Boolean Algebra

**Chapter 3 : Logic Gates, Logic Circuits and
Digital Integrated Circuits**

Chapter 3

Logic Gates, Logic Circuits and Digital Integrated Circuits

3.1 Logic Gates

- + Electronic switches and Logic Levels in Digital Circuits
- + Basic Logic Gates

3.2 Logic Circuits


- + Principles of Logic Gate Connection
- + Two models of Logic Circuit
- + Synthesis and Analysis Logic Circuits
- + Active Level and Active Level Conversion

3.3 Digital Integrated Circuits

- + Integrated Circuit (IC) and Scale of Integration.
- + Digital IC Families (TTL, CMOS)
- + Specifications of Digital IC

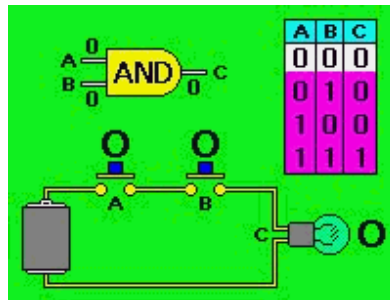3.1 LOGIC GATES

✓ Digital circuits work with 0 and 1 and use “switches”




Ref.: <http://www.wordbench.com/video/ucan.html>


How to make an electronic “switch” in digital circuit ?.

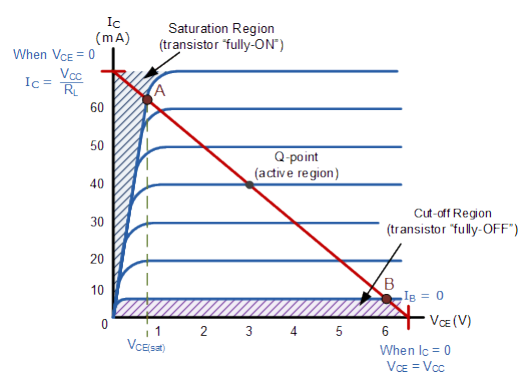3.1 LOGIC GATES

✓ BJT works as a switch in a digital circuits




BJT switches → **TTL families**

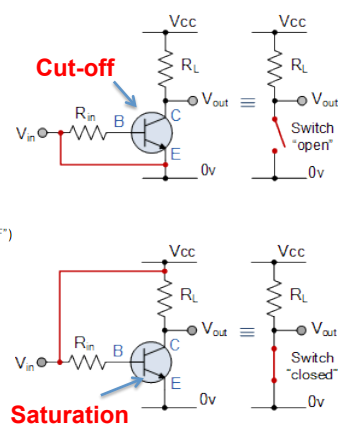

Ref.: http://www.electronics-tutorials.ws/transistor/tran_4.html

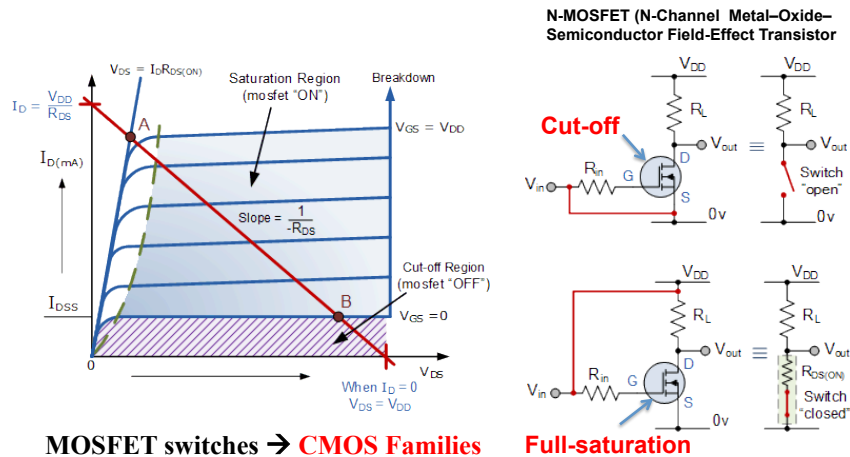3.1 LOGIC GATES

✓ MOSFET works as a switch in a digital circuits



MOSFET switches → CMOS Families


Ref.: http://www.electronics-tutorials.ws/transistor/tran_4.html

Dr. Le Dung - School of Electronics and Telecommunications

Page 7

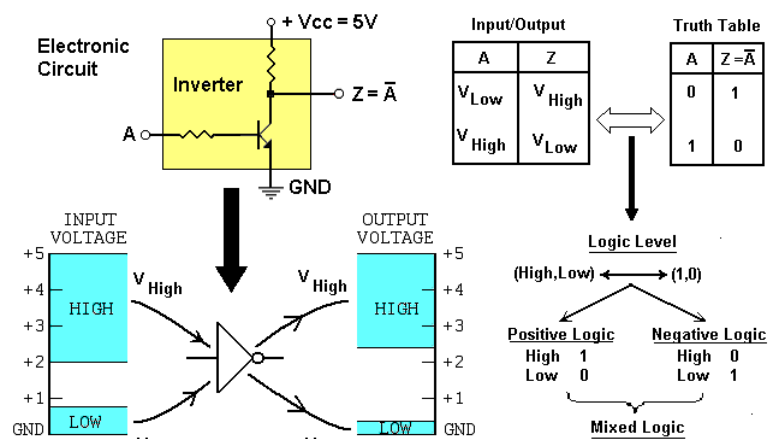3.1 LOGIC GATES

✓ Logic Levels: are usually represented by the **voltage ranges**.




Dr. Le Dung - School of Electronics and Telecommunications

Page 8

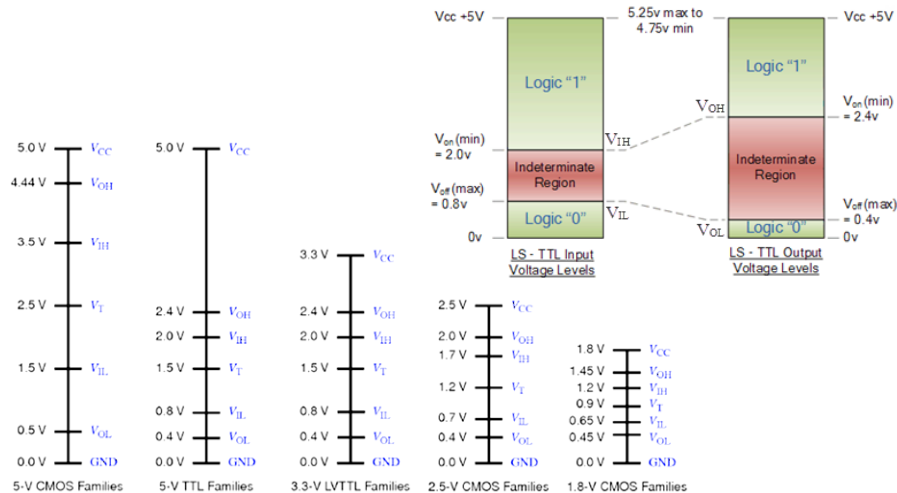3.1 LOGIC GATES

✓ Logic Levels: V_{CC} , V_{IH} , V_{IL} , V_{OH} , V_{OL}




Dr. Le Dung - School of Electronics and Telecommunications


Page 9

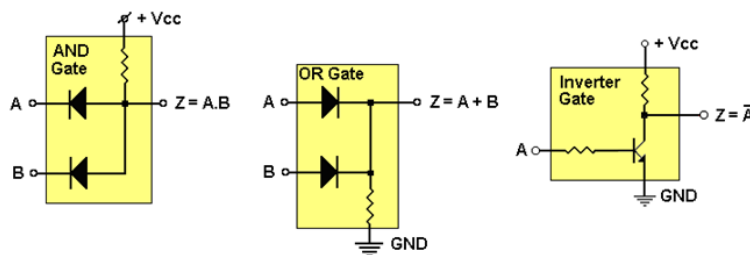3.1 LOGIC GATES

✓ A Logic Gate is physical device implementing a basic Boolean function and working on logic levels.



Logic gates are primarily implemented using diodes or transistors acting as electronic switches

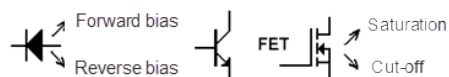
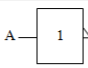

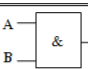

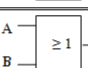



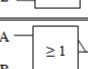

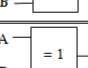

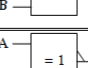


Dr. Le Dung - School of Electronics and Telecommunications

Page 10

3.1 LOGIC GATES



✓ 7 Logic Gates

LOGIC GATE	TRADITIONAL LOGIC SYMBOL	IEEE/ANSI LOGIC SYMBOL	FUNCTION	TRUTH TABLE		
				INPUT		OUTPUT
INVERTER (NOT)			$Z = \overline{A}$	B	A	Z
				0	1	0
AND			$Z = A \cdot B$	0	0	0
				0	1	0
				1	0	0
				1	1	1
OR			$Z = A + B$	0	0	0
				0	1	1
				1	0	1
				1	1	1
NAND			$Z = \overline{A \cdot B}$	0	0	1
				0	1	1
				1	0	1
				1	1	0
NOR			$Z = \overline{A + B}$	0	0	1
				0	1	0
				1	0	0
				1	1	0
XOR			$Z = A \oplus B$	0	0	0
				0	1	1
				1	0	1
				1	1	0
XNOR			$Z = A \sim B$ $= A \oplus B$	0	0	1
				0	1	0
				1	0	0
				1	1	1


3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Hex (6) Inverters IC 7404

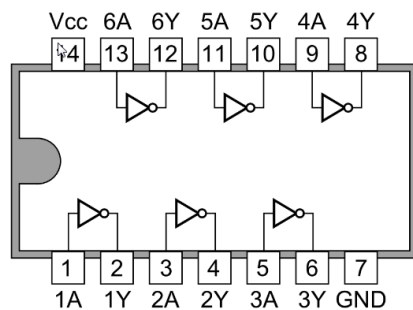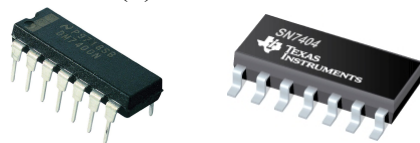

INVETER gate

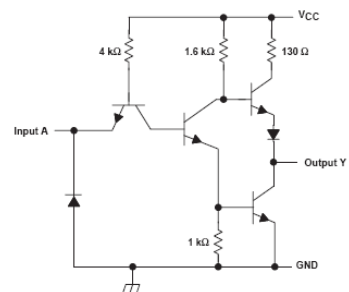




TTL inverter gate circuit

3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Quadruple 2-Input And-gates IC 7408

AND gate

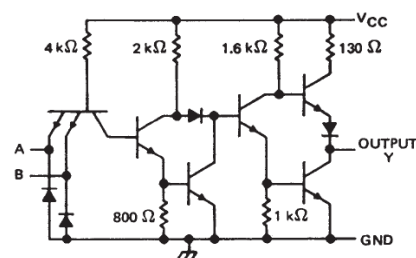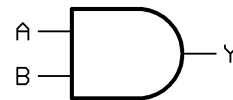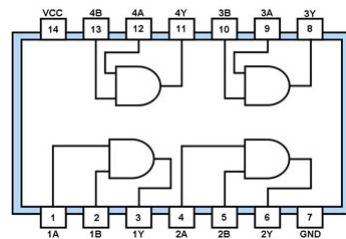




TTL AND gate circuit

3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Quadruple 2-Input OR-gates IC 7432

OR gate

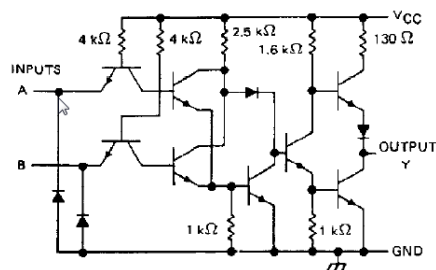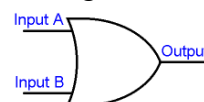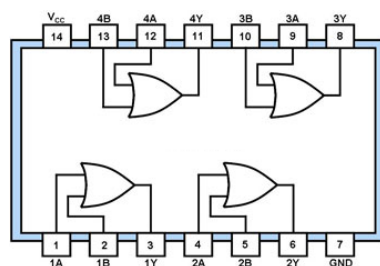



TTL OR gate circuit

3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Quadruple 2-Input NAND-gates IC 7400

NAND gate

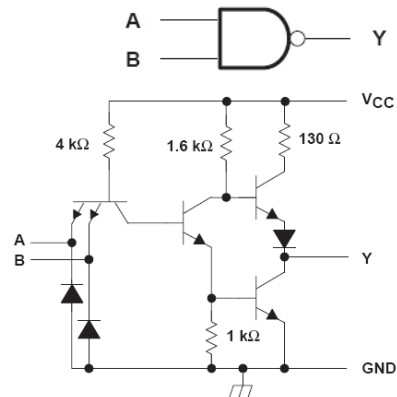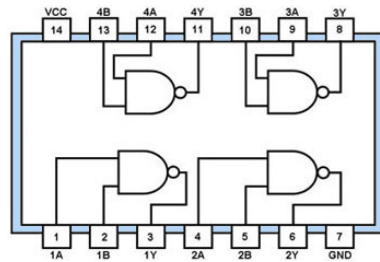



TTL NAND gate circuit

3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Quadruple 2-Input NOR-gates IC 7402

NOR gate


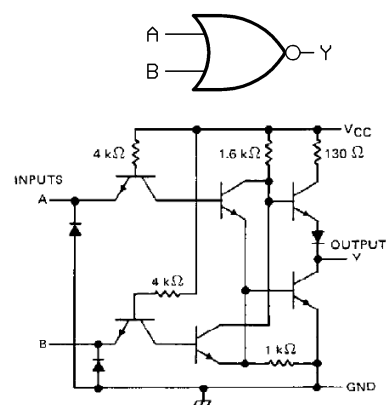
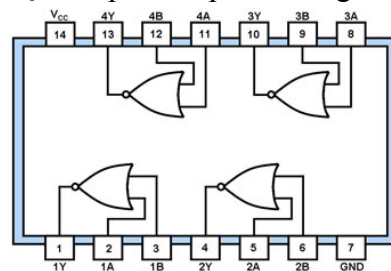


TTL NOR gate circuit

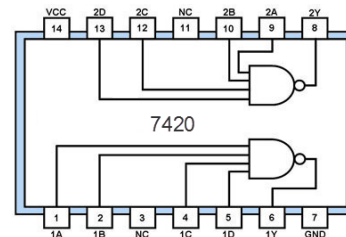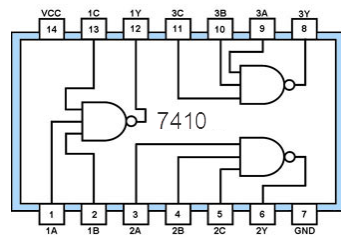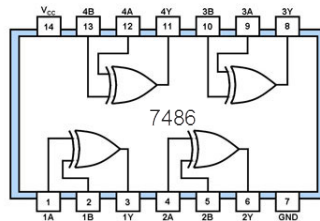3.1 LOGIC GATES

✓ Logic Gates in Small Scale Integrated IC

Quad 2-Input Exclusive-Or Gates: 7486, 74136




Dr. Le Dung - School of Electronics and Telecommunications

Page 17

3.2 LOGIC CIRCUITS

✓ Principles of Logic Gate Connection

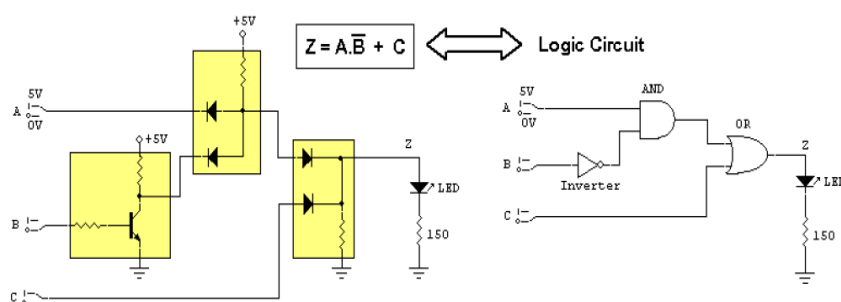

The rules of connection ?.


Dr. Le Dung - School of Electronics and Telecommunications

Page 18

3.2 LOGIC CIRCUITS

✓ Principles of Logic Gate Connection

e.g. TTL output connects to CMOS input

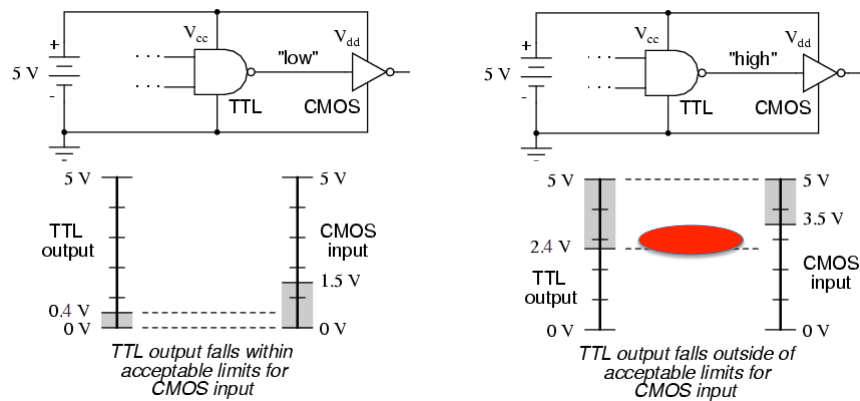


3.2 LOGIC CIRCUITS

✓ Principles of Logic Gate Connection → **the rules**

- + Must be compatible in logic level
- + One output can control more than one input
- + Two or more outputs usually should not be connected together.
- + Don't let an input as a floating input.


3.2 LOGIC CIRCUITS

✓ Two models of Logic Circuits

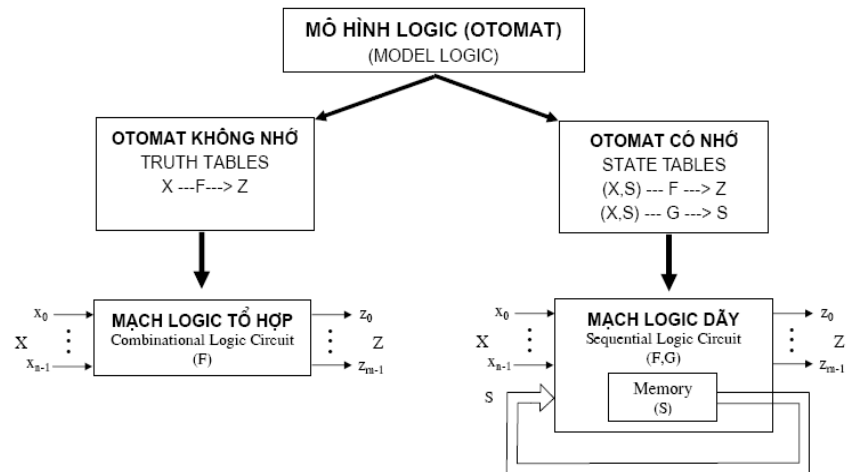


3.2 LOGIC CIRCUITS

✓ Synthesis and Analysis Logic Circuits

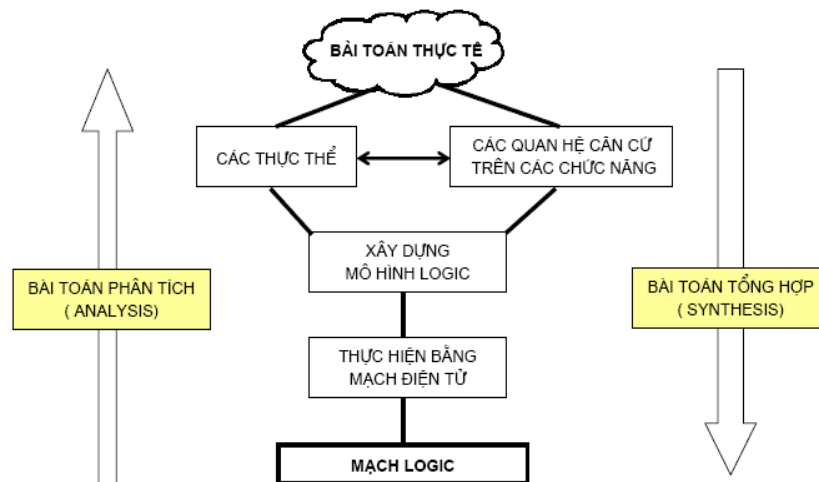


3.2 LOGIC CIRCUITS

✓ Active Level (Asserted level)

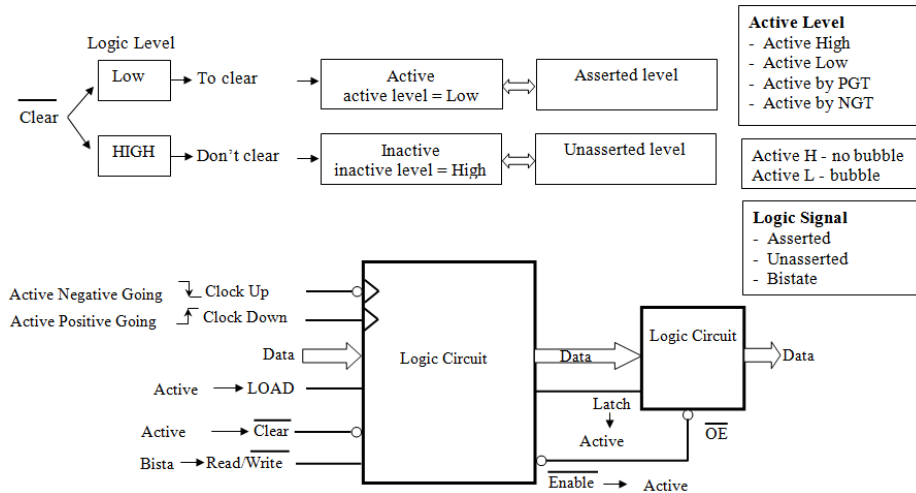






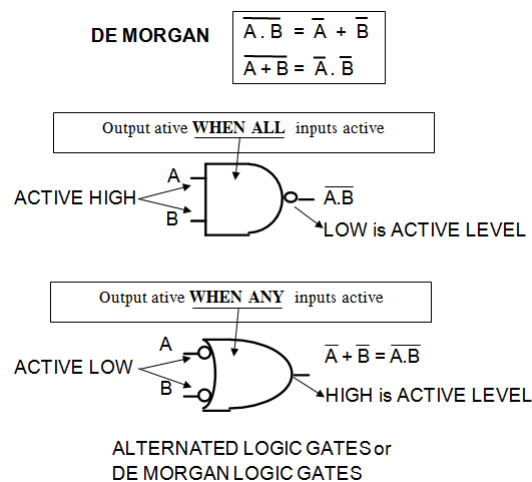




3.2 LOGIC CIRCUITS

✓ Active Level Conversion

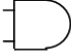


3.2 LOGIC CIRCUITS

✓ Alternated Logic Gates (active level conversion)

GATE	STANDARD LOGIC GATES	ALTERNATED LOGIC GATES
INV		
AND		
OR		
NAND		
NOR		

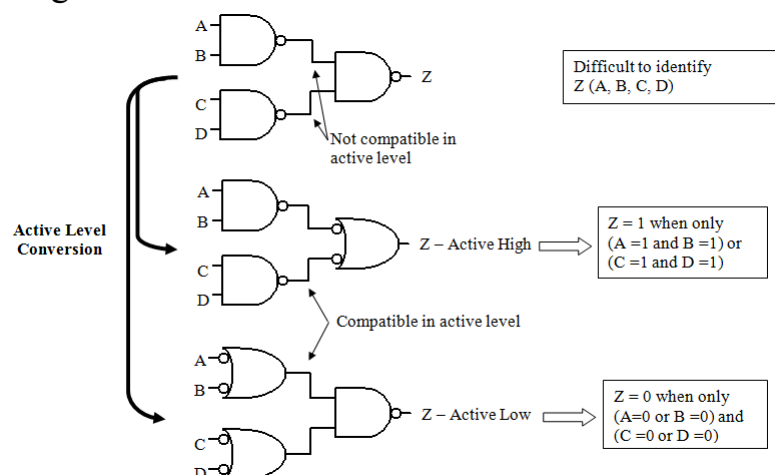3.2 LOGIC CIRCUITS


✓ Active level conversion to make a compatible in logic circuits



3.2 LOGIC CIRCUITS

✓ Exercise 1: active level conversion


Floppy Driver Controller

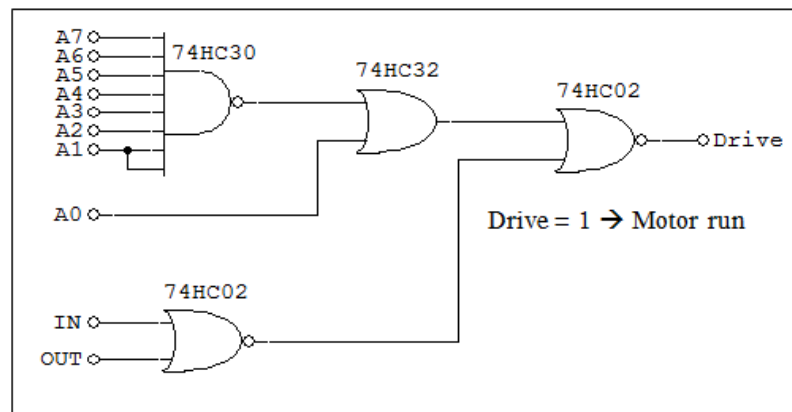

3.2 LOGIC CIRCUITS

✓ Exercise 2: active level conversion


Memory Access Controller

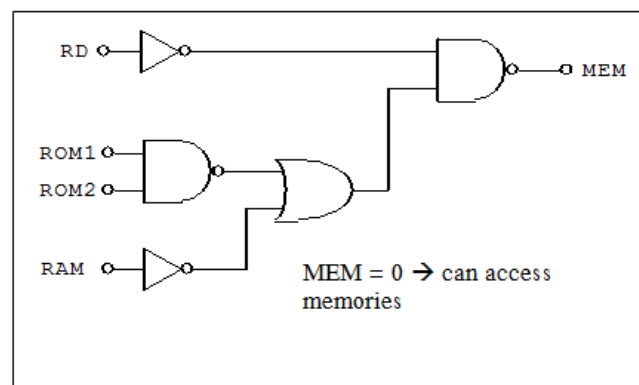

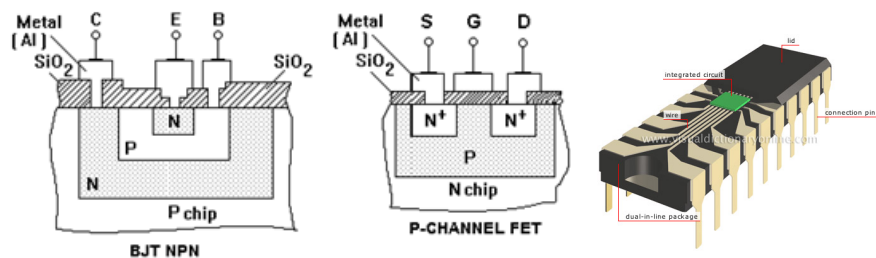3.3 DIGITAL INTEGRATED CIRCUITS

✓ Integrated Circuit ?.


An integrated circuit (also referred to as IC, chip, or microchip) is an electronic circuit manufactured by **lithography**



All logic gates, logic circuits → implemented on a single chip → **Digital ICs**

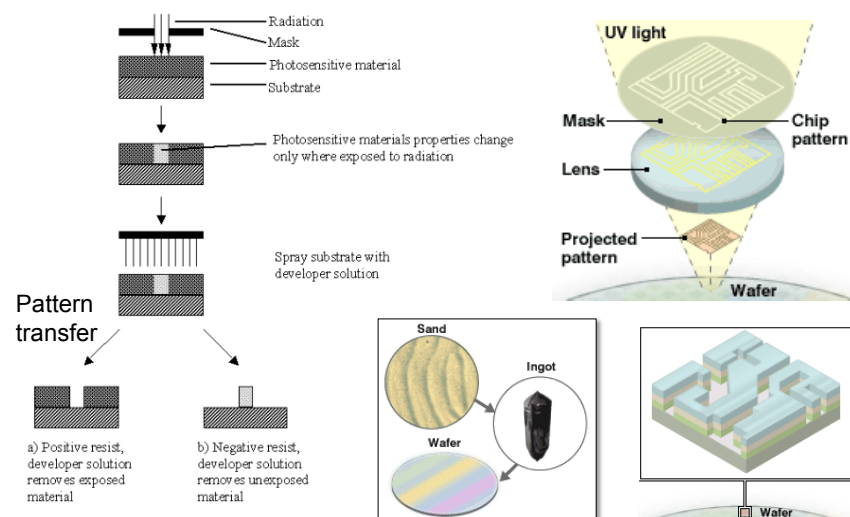3.3 DIGITAL INTEGRATED CIRCUITS

✓ Lithography for integrated circuit fabrication



3.3 DIGITAL INTEGRATED CIRCUITS

✓ Scale of Integration

SCALE OF INTEGRATION	NUMBER OF GATES	APPLICATION
SSI <i>Small-Scale Integrated</i>	< 12	"Off-the-shelf" IC for basic logic gate and Flip-flop
MSI <i>Medium-Scale Integrated</i>	12 ~ 99	"Off-the-shelf" IC Decoder, Encoder, Mux, Counter, Shift registers
LSI <i>Large-Scale Integrated</i>	100 ~ 9999	A digital system, such as digital clock, calculator, memory RAM ROM, PROM, EPROM, Flash, Microcontroller, Microprocessors, System on Chip ...
VLSI <i>Very-Large-Scale Integrated</i>	10,000 ~ 99,999	
ULSI <i>Ultra-Large-Scale Integrated</i>	> 100,000	

* Giga-scale integration(GSI) 1,000,000 or more($10^9 - 10^{11}$)

* Tera-scale integration(TSI) (10^{12} or more)

1.2 Billion individual transistor gates onto the Quad-core i7-2700k "Sandy Bridge" 64-bit microprocessor chip

Moore's Law: The number of components that can be packed on a computer chip doubles every 18 months while price stays the same.

3.3 DIGITAL INTEGRATED CIRCUITS

✓ Most of the reasons that modern digital systems use integrated circuits

- ❖ IC pack a lot more circuitry in a small package → the overall size of any digital system is reduced.
- ❖ IC have made digital systems more reliable by reducing the number of external interconnections.
- ❖ IC typically requires less power than their discrete counterparts → saving in power and a system does not require as much cooling

3.3 DIGITAL INTEGRATED CIRCUITS

✓ Logic Families

DL : Diode Logic.

RTL : Resistor Transistor Logic.

DTL : Diode Transistor Logic.

HTL : High Threshold Logic.

TTL : **Transistor Transistor Logic.**


I²L : Integrated Injection Logic.

ECL : Emitter Coupled Logic.

MOS : Metal Oxide Semiconductor Logic (PMOS and NMOS).

CMOS : **Complementary Metal Oxide Semiconductor Logic.**

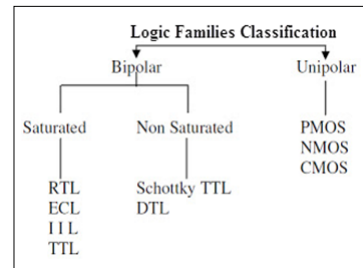BiCMOS : Combines bipolar and CMOS devices into single integrated circuit.



3.3 DIGITAL INTEGRATED CIRCUITS

✓ Digital IC notation



DM 74 LS 08 N


Manufacture Code —> DM
Type 74 (54) —> 74
Logic Family —> LS
Package —> N
Function —> 08



TTL	Ha CMOS
None = Standard TTL	C = compatible with 74 TTL.
ALS = Advanced Low-power Schottky TTL logic.	HC = High-speed CMOS with V _{cc} = from +2V to 6V.
AS = Advanced Schottky TTL logic.	FACT- Fairchild Advanced CMOS Technology
F = FACT Fairchild Advanced Schottky TTL logic.	<u>Includes:</u>
H = High-speed TTL logic.	74AC, 74ACQ, 74ACT, 74ACTQ, 74FCT, 74FCTA, 74HCT
L = Low-power TTL logic.	
LS = Low-power Schottky TTL logic.	
S = Schottky TTL logic.	

3.3 DIGITAL INTEGRATED CIRCUITS

✓ DL, RTL, DTL, HTL structures

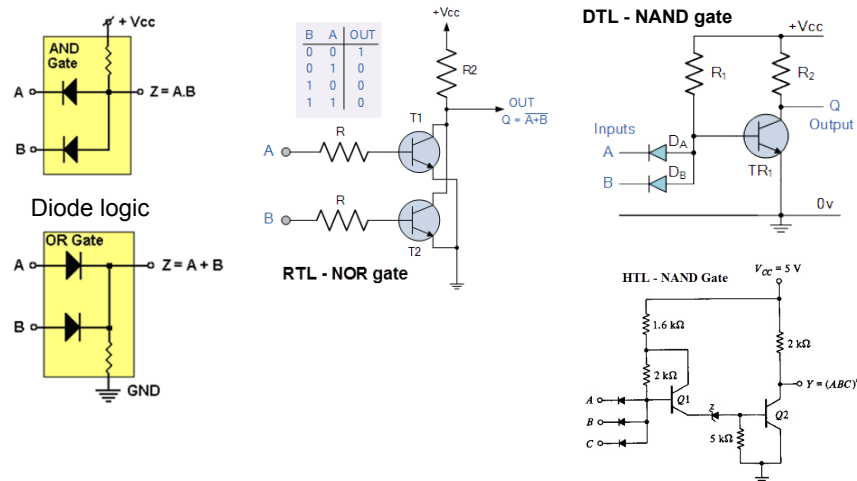


Dr. Le Dung - School of Electronics and Telecommunications

Page 35

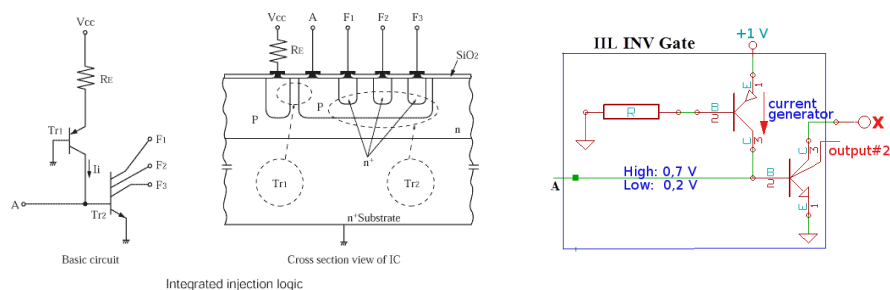3.3 DIGITAL INTEGRATED CIRCUITS

✓ IIL structures

- Integrated injection logic (IIL, I2L, or I2L) is a class of digital circuits built with multiple collector bipolar junction transistors (BJT)
- When introduced it had speed comparable to TTL yet was almost as low power as CMOS, making it ideal for use in VLSI (and larger) integrated circuits.
- Although the logic voltage levels are very close (High: 0.7V, Low: 0.2V),




Dr. Le Dung - School of Electronics and Telecommunications

Page 36

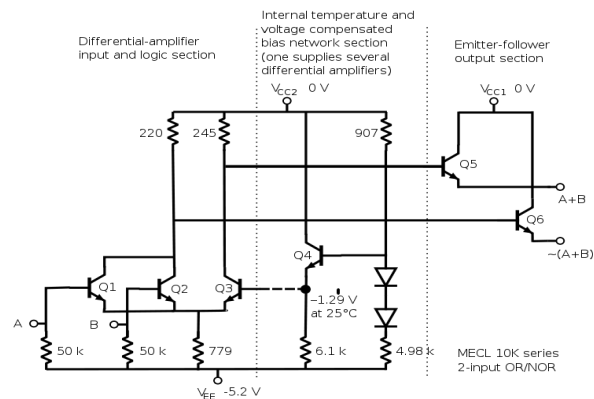3.3 DIGITAL INTEGRATED CIRCUITS

✓ ECL structures


- A high-speed integrated circuit bipolar transistor logic family.
- ECL uses an overdriven BJT differential amplifier with single-ended input and limited emitter current to avoid the saturated (fully on) region of operation and its slow turn-off behavior



3.3 DIGITAL INTEGRATED CIRCUITS


✓ The structure of standard TTL NAND Gate:

Multiple emitter and Totem pole

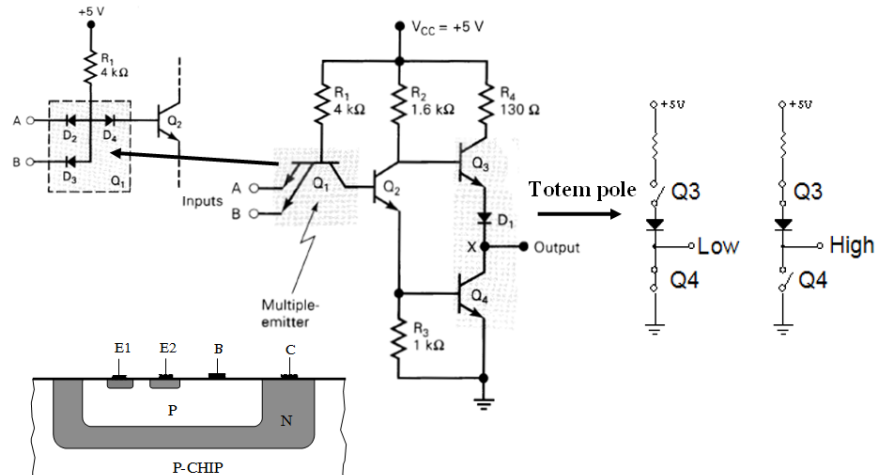

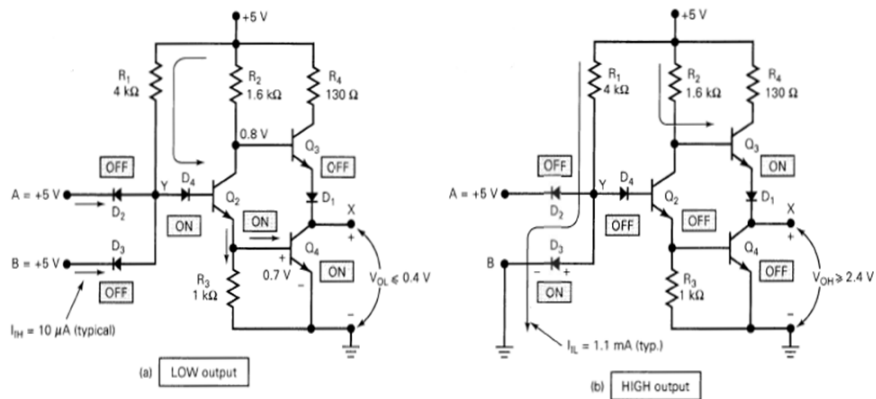
3.3 DIGITAL INTEGRATED CIRCUITS

✓ The operation of standard TTL NAND gate



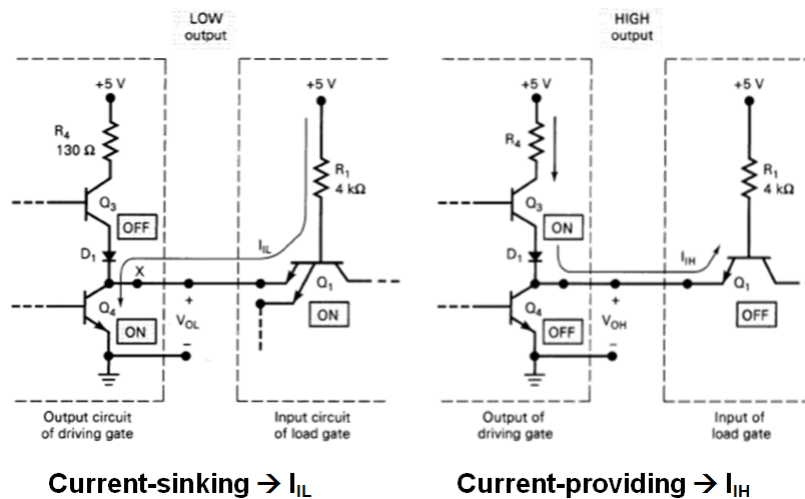
3.3 DIGITAL INTEGRATED CIRCUITS

✓ The operation of standard TTL NAND gate




3.3 DIGITAL INTEGRATED CIRCUITS

✓ Tri-state or Hi-Z output of TTL gate

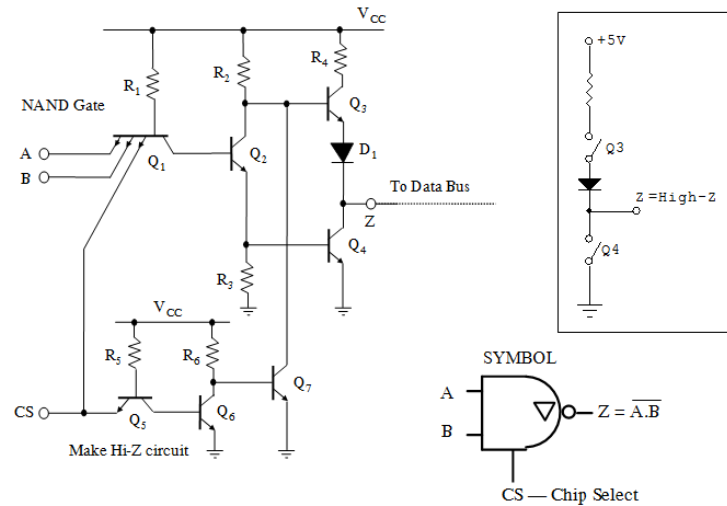


3.3 DIGITAL INTEGRATED CIRCUITS

✓ Tri-states output application

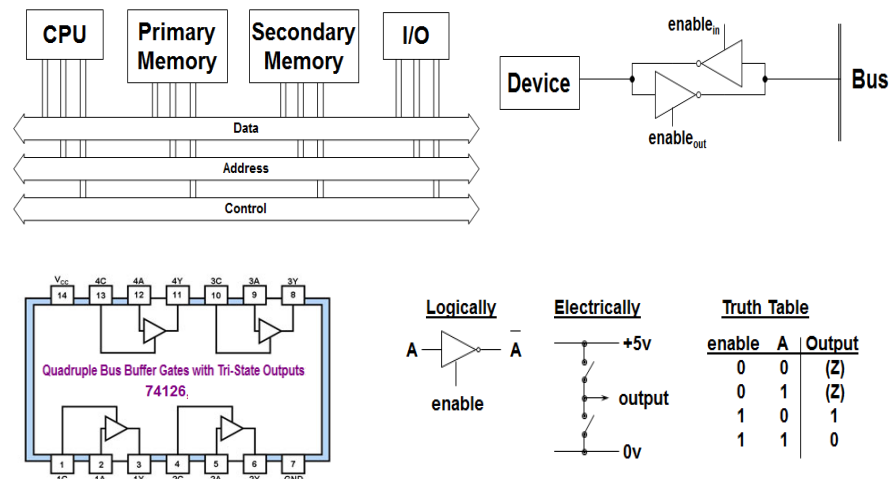


3.3 DIGITAL INTEGRATED CIRCUITS

✓ Open collector output of TTL gate

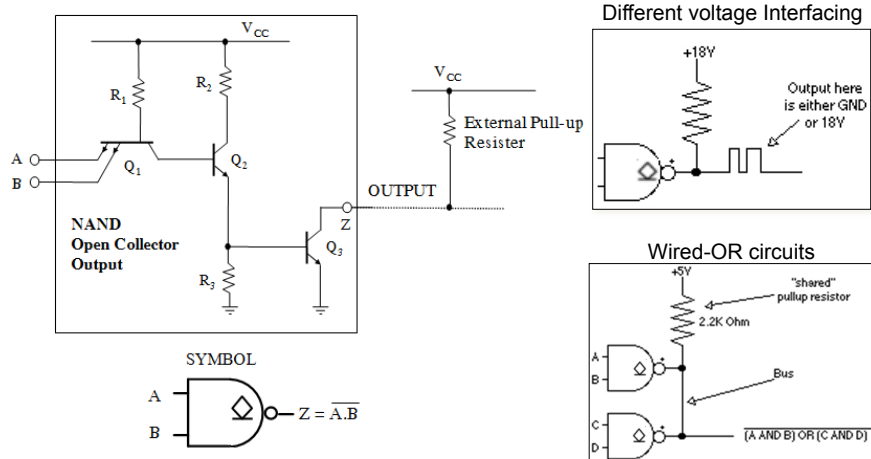


3.3 DIGITAL INTEGRATED CIRCUITS

✓ Structure of Low-power Schottky TTL

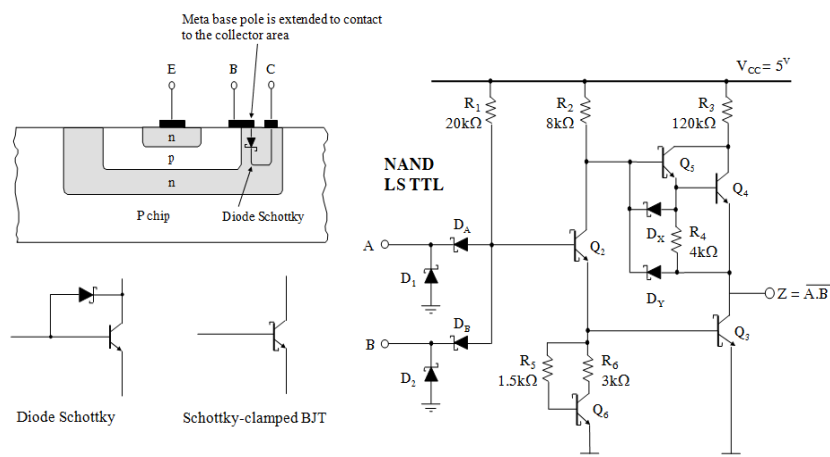


3.3 DIGITAL INTEGRATED CIRCUITS

✓ Structure of NMOS gate

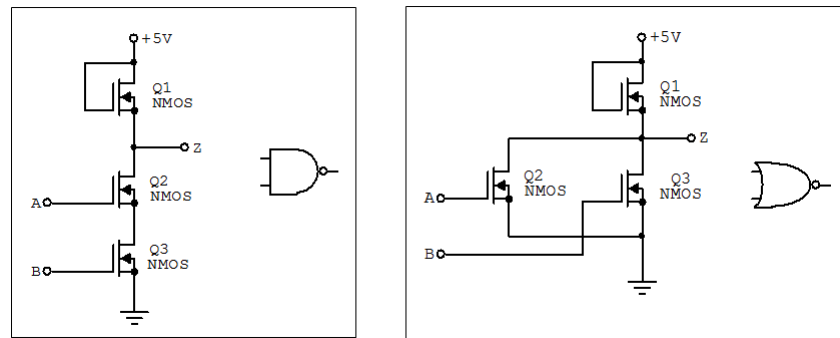

3.3 DIGITAL INTEGRATED CIRCUITS


✓ Structure of CMOS gate

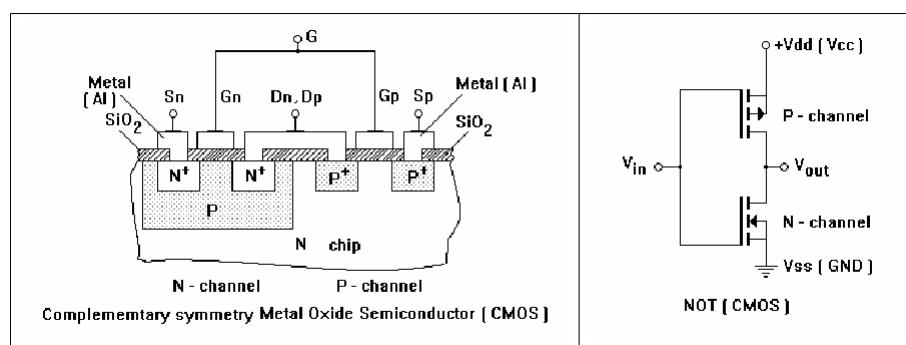

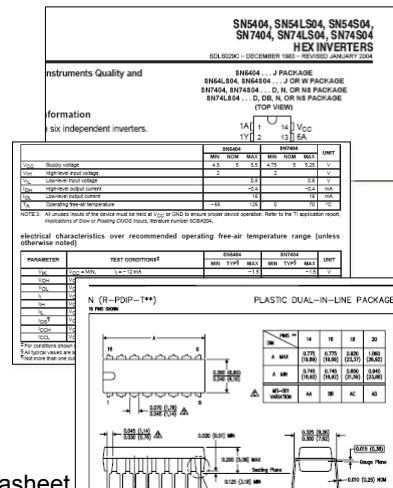3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC

- Currents & Voltages
- Fan-out, Fan-in
- Propagation Delay
- Noise Margin
- Power Dissipation
- Speed Power Product



From Datasheet



3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC

➤ Voltages and Noise Margin

- $V_{IH(min)}$ The minimum voltage level at the input to be recognised as H.
- $V_{IL(max)}$ The maximum voltage level at the input to be recognised as L.
- $V_{OH(min)}$ The minimum voltage at the output when in state H.
- $V_{OL(max)}$ The maximum voltage at the output when in state L.
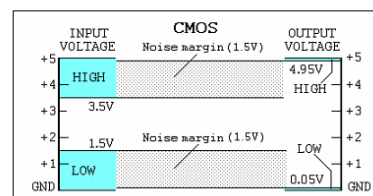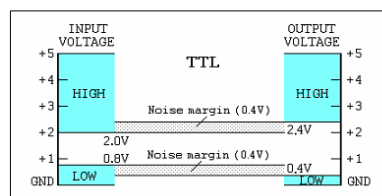
$$\text{Condition} \quad \begin{cases} V_{OH(min)} \geq V_{IH(min)} \\ V_{OL(max)} \leq V_{IL(max)} \end{cases}$$




3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC

➤ Currents & Fan-out, Fan-in

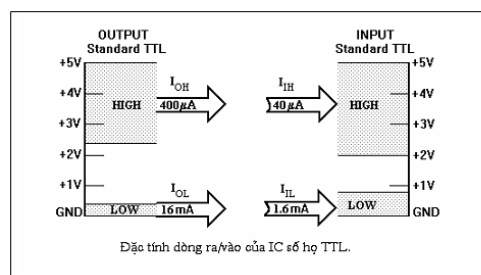- I_{IH} The current flowing into the input when a specified H voltage is applied.
- I_{IL} The current flowing into the input when a specified L voltage is applied.
- I_{OH} The current flowing out of the output when in state H.
- I_{OL} The current flowing out of the output when in state L.



$$\text{FANOUT} = \min \left(\frac{|I_{OH}|}{|I_{IH}|}, \frac{|I_{OL}|}{|I_{IL}|} \right)$$

e.g.: Standard TTL
FANOUT = 10

3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC


➤ Currents of the logic families

LOGIC FAMILY		OUTPUT	INPUT
TTL	Standard TTL	$I_{OH} = 400 \mu A$ $I_{OL} = 16 \text{ mA}$	$I_{IH} = 40 \mu A$ $I_{IL} = 1.6 \text{ mA}$
	Low Power Schottky (LS)	$I_{OH} = 400 \mu A$ $I_{OL} = 8 \text{ mA}$	$I_{IH} = 20 \mu A$ $I_{IL} = 400 \mu A$
	Advanced Low Power Schottky (ALS)	$I_{OH} = 400 \mu A$ $I_{OL} = 8 \text{ mA}$	$I_{IH} = 20 \mu A$ $I_{IL} = 100 \mu A$
	FAST Fairchild Advanced Schottky TTL (F)	$I_{OH} = 1 \text{ mA}$ $I_{OL} = 20 \text{ mA}$	$I_{IH} = 20 \mu A$ $I_{IL} = 0.6 \text{ mA}$
CMOS	4000 Series	$I_{OH} = 400 \mu A$ $I_{OL} = 400 \mu A$	$I_{ia} = 1 \mu A$
	74HC00 Series	$I_{OH} = 4 \text{ mA}$ $I_{OL} = 4 \text{ mA}$	$I_{ia} = 1 \mu A$
	FAST Fairchild Advanced CMOS Technology Series (AC/ACT/ACQ/ACTQ)	$I_{OH} = 24 \text{ mA}$ $I_{OL} = 24 \text{ mA}$	$I_{ia} = 1 \mu A$
	FAST Fairchild Advanced CMOS Technology Series (FCT/FCTA)	$I_{OH} = 15 \text{ mA}$ $I_{OL} = 64 \text{ mA}$	$I_{ia} = 1 \mu A$

3.3 DIGITAL INTEGRATED CIRCUITS


✓ Specifications of Digital IC

➤ Propagation Delay

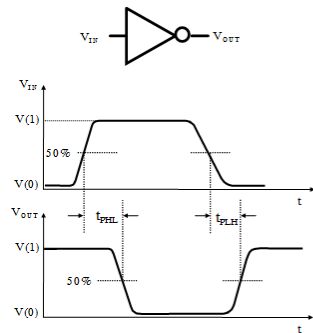

- t_{PLH} Time taken to go from L to H.
- t_{PHL} Time taken to go from H to L.
- The average propagation delay is

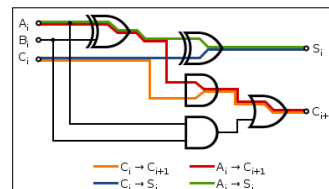
$$t_{P(ave)} = \frac{t_{PLH} + t_{PHL}}{2}$$



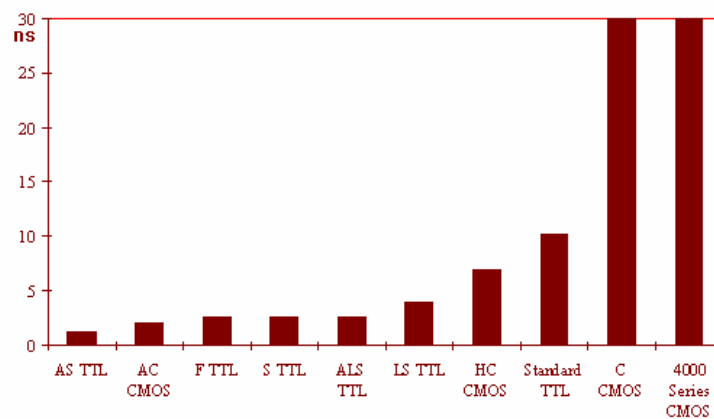3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC


➤ Propagation delay of the TTL and CMOS families



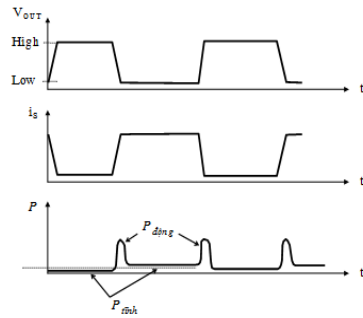3.3 DIGITAL INTEGRATED CIRCUITS

✓ Specifications of Digital IC

➤ Power Dissipation and Speed-Power Product



I_{CCH} The current when all gate outputs in the High.

I_{CCL} The current when all gate outputs in the Low.

The average current drawn is

$$I_{CC(ave)} = \frac{I_{CCH} + I_{CCL}}{2}$$

Therefore the **average power** consumed is

$$P_{D(ave)} = I_{CC(ave)} \times V_{CC}$$


SPEED-POWER PRODUCT

$$DP = t_D P_D \text{ (watt-second) } \rightarrow \text{picojoules (pJ)}$$

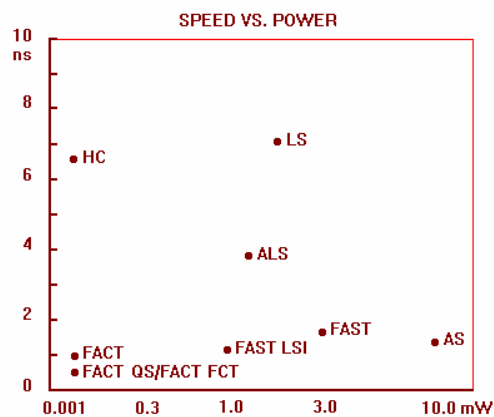3.3 DIGITAL INTEGRATED CIRCUITS


✓ Specifications of Digital IC

➤ Speed and power dissipation of TTL and CMOS families




3.3 DIGITAL INTEGRATED CIRCUITS

✓ TTL and CMOS connections

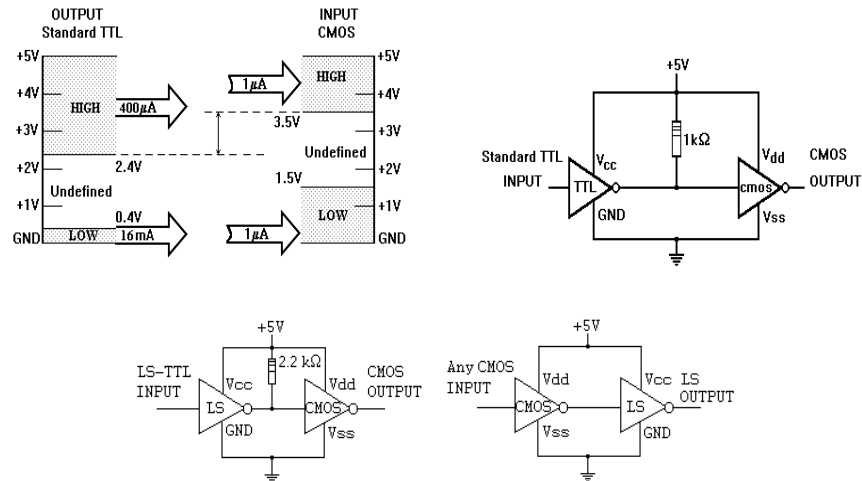


3.3 DIGITAL INTEGRATED CIRCUITS

✓ TTL and CMOS connections (cont.)

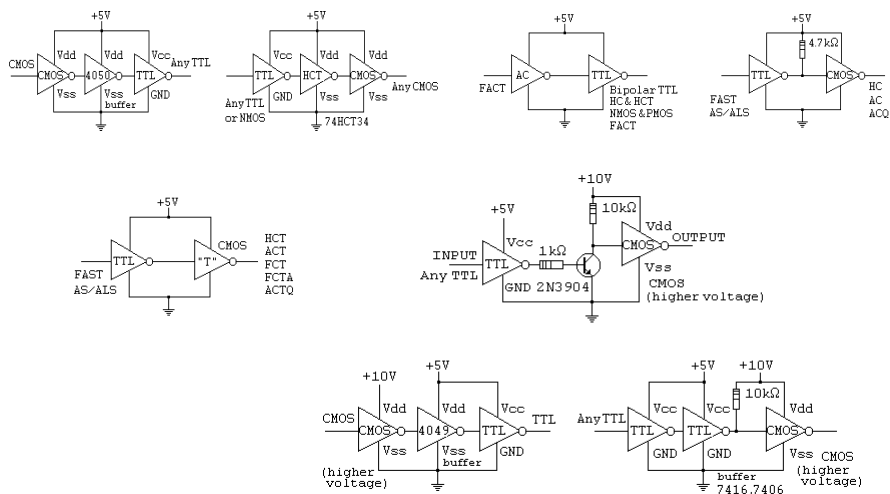

3.3 DIGITAL INTEGRATED CITCUITS

✓ TTL and CMOS connect to LED

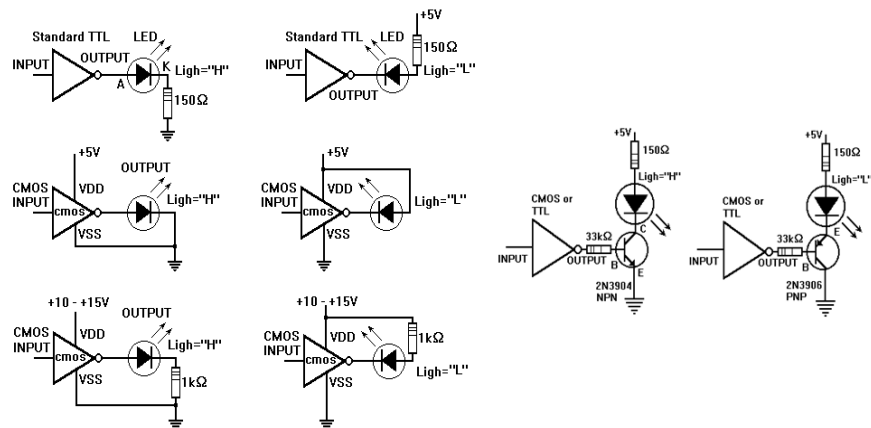

3.3 DIGITAL INTEGRATED CITCUITS

✓ TTL and CMOS connect to a push button or a relay

